

Tutorial of Derivation of Inverter Transfer Function

1. Filter Analysis

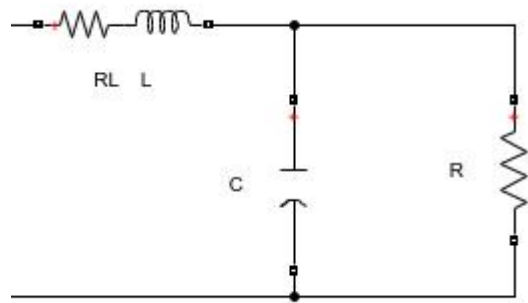


Fig.1 Equivalent circuit of inverter filter

KVL Law's:

$$(1) V_{in} = L \frac{di}{dt} + i_L R_L + V_o$$

$$(2) C \frac{dV_C}{dt} = i_L - i_{out}$$

1.1 Output Voltage Version

After Laplace Transfer:

$$(3) V_{in} = Li_L s + i_L R_L + V_o$$

$$(4) i_L = \frac{V_o}{R} + CV_o s \quad (V_C = V_o)$$

By substituting the value of i_L in (3)

$$V_{in} = (Ls + R_L) \left(\frac{V_o}{R} + CV_o s \right) + V_o$$

So

$$V_{in} = V_o \left[CLs^2 + \left(\frac{L}{R} + CR_L \right) s + \frac{R + R_L}{R} \right]$$

1.2 Output Current Version

After Laplace Transfer:

$$(5) V_{in} = Li_L s + i_L R_L + i_o R$$

$$(6) i_L = i_o (CRs + 1)$$

By substituting the value of i_L in (5)

$$V_{in} = Li_o (CRs + 1)s + i_o (CRs + 1)R_L + i_o R$$

So

$$V_{in} = i_o [LCRs^2 + (L + CRR_L)s + R + R_L]$$

1.3 Inverter Current Version

After Laplace Transfer:

$$(7) V_{in} = Li_L s + i_L R_L + i_o R$$

$$(8) i_o = \frac{i_L}{(CRs+1)}$$

By substituting the value of i_o in (7)

$$V_{in} = Li_L s + i_L R_L + \frac{i_L R}{CRs + 1}$$

So

$$V_{in} = i_L (Ls + R_L + \frac{R}{CRs + 1})$$

2. PWM Analysis

$$G_{PWM}(s) = \frac{V_x(s)}{m(s)} [m(s) \text{ is Modulation signal}]$$

$$G_{PWM}(s) = \frac{1}{C_{pk}} * \frac{1 - s \frac{T_s}{4}}{1 + s \frac{T_s}{4}} 2V_{DC}$$

The duty ratio, which is the fraction of time in a cycle that the single update modulating signal ($m(s)$) is higher than the triangle carrier, can be expressed by the value of a single update modulating signal in a cycle to the peak of triangle carrier (C_{pk}).

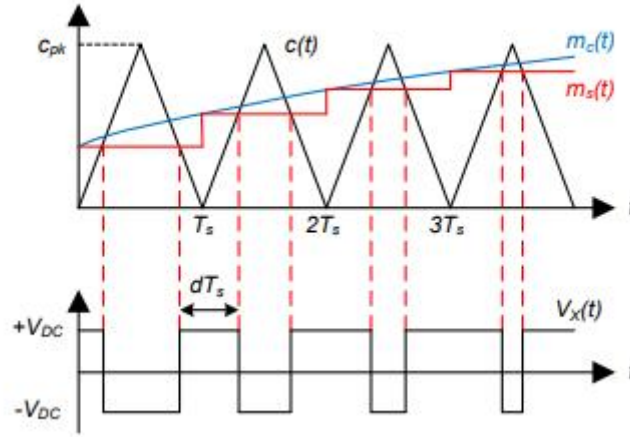


Fig.2 Single update PWM with triangle carrier

3. Summary

3.1 Output Voltage Version

$$G_{PWM}(s)m(s) = V_o [CLs^2 + (\frac{L}{R} + CR_L)s + \frac{R+R_L}{R}] (V_x=V_{in})$$

So the transfer function of modulation signal and output voltage

$$\frac{V_o}{m} = \frac{G_{PWM}(s)}{LCs^2 + \left(\frac{L}{R} + CR_L\right)s + \frac{R + R_L}{R}}$$

3.2 Output Current Version

$$G_{PWM}(s)m(s) = i_o[LCRs^2 + (L + CRR_L)s + R + R_L]$$

So the transfer function of modulation signal and output current

$$\frac{i_o}{m} = \frac{G_{PWM}(s)}{LCs^2 + \left(\frac{L}{R} + CR_L\right)s + \frac{R + R_L}{R}}$$

3.3 Inverter Current Version

$$G_{PWM}(s)m(s) = i_L(Ls + R_L + \frac{R}{CRs + 1})$$

So the transfer function of modulation signal and inverter current

$$\frac{i_L}{m} = \frac{Cs + \frac{1}{R}}{LCs^2 + \left(\frac{L}{R} + CR_L\right)s + \frac{R + R_L}{R}} G_{PWM}(s)$$